


CprE 381, Computer Organization and Assembly-Level Programming

Lab 2 Report

Student Name _____Michael Mota_____

Submit a typeset pdf version of this on Canvas by the due date. Refer to the highlighted language in the lab document for the context of the following questions.

 
[Part 3 (a)] Draw the interface description (i.e., the “symbol” or high-level blackbox) for the RISC-V register file. Which ports do you think are necessary, and how wide (in bits) do they need to be?



We need a clock input which is 1 bit because writes happen on a clock edge, plus a write-enable (1 bit) to tell the register file when to actually write. We also need three 5-bit address inputs—rs1, rs2, and rd—since 5 bits selects one of 32 registers, and a 32-bit wdata input for what you’re writing. Finally, we need two 32-bit outputs, one for the rs1 read data and one for the rs2 read data.

[Part 3 (b)] Create an N-bit register using this flip-flop as your basis.

[Part 3 (c)] Waveform.

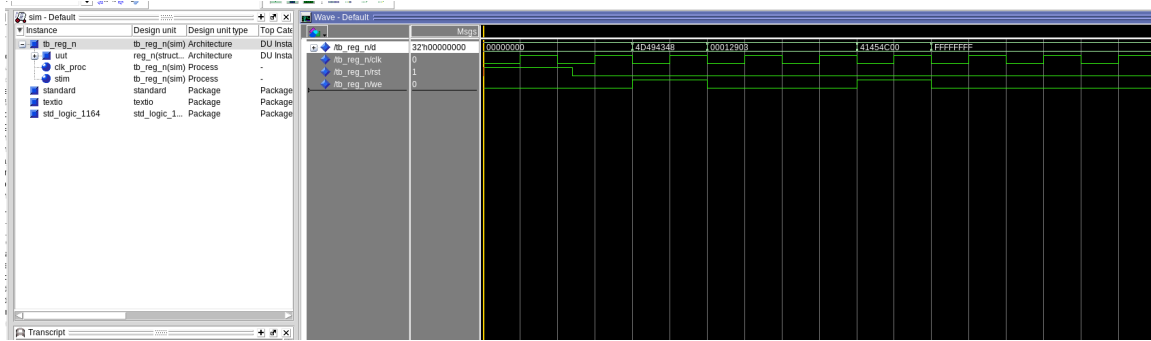


reate a testbench to test your register design to make sure it is working as expected, and include a waveform screenshot in your report PDF. A sample testbench that also incorporates a clock generator can be found in tb_dff.vhd. [You will need to modify this slightly for your N-bit version.]

[Part 3 (d)] What type of decoder would be required by the RISC-V register file and why?

For a riscv register file you need a 5-to-32 (5:32) decoder because the RISC-V register file has 32 registers, and a register index like rd is 5 bits (since $2^5 = 32$). The decoder turns that 5-bit rd value into a one-hot 32-bit write-enable bus so only the selected register gets written.


[Part 3 (e)] **Waveform.**

 

This waveform is showing your 5-to-32 decoder doing the one-hot thing: when the 5-bit input changes (like 00, 01, 1F), the 32-bit output jumps so exactly one bit is '1' (ex: 00 -> 00000001, 01 -> 00000002, 1F -> 80000000).


[Part 3 (f)] In your write-up, describe and defend the design you intend on implementing for the next part. For the register-file read path, i will implement the 32-bit 32:1 mux as a dataflow component using a single combinational selection statement (e.g., with `i_S select o_Y <= ...` or an equivalent case in a combinational process). This approach is compact, easy to verify in simulation, and synthesizes efficiently into the same kind of mux structure a structural "tree of 2:1 muxes" would produce, without the coding overhead. Since reads must be available immediately (no clocked behavior), a purely combinational dataflow mux is the most appropriate choice for selecting one 32-bit register output from the 32 parallel register outputs.

[Part 3 (g)] **Waveform.**

 


In this waveform, we verify the behavior of our 32-bit 32:1 multiplexer. The wide upper signal represents the concatenated set of 32 possible 32-bit inputs, the middle signal is the 5-bit select value, and the lower signal is the 32-bit output. As we vary the select (e.g., 0, 1, 9, 31), the output updates immediately to the corresponding 32-bit slice, demonstrating the expected purely combinational selection used for register-file reads.

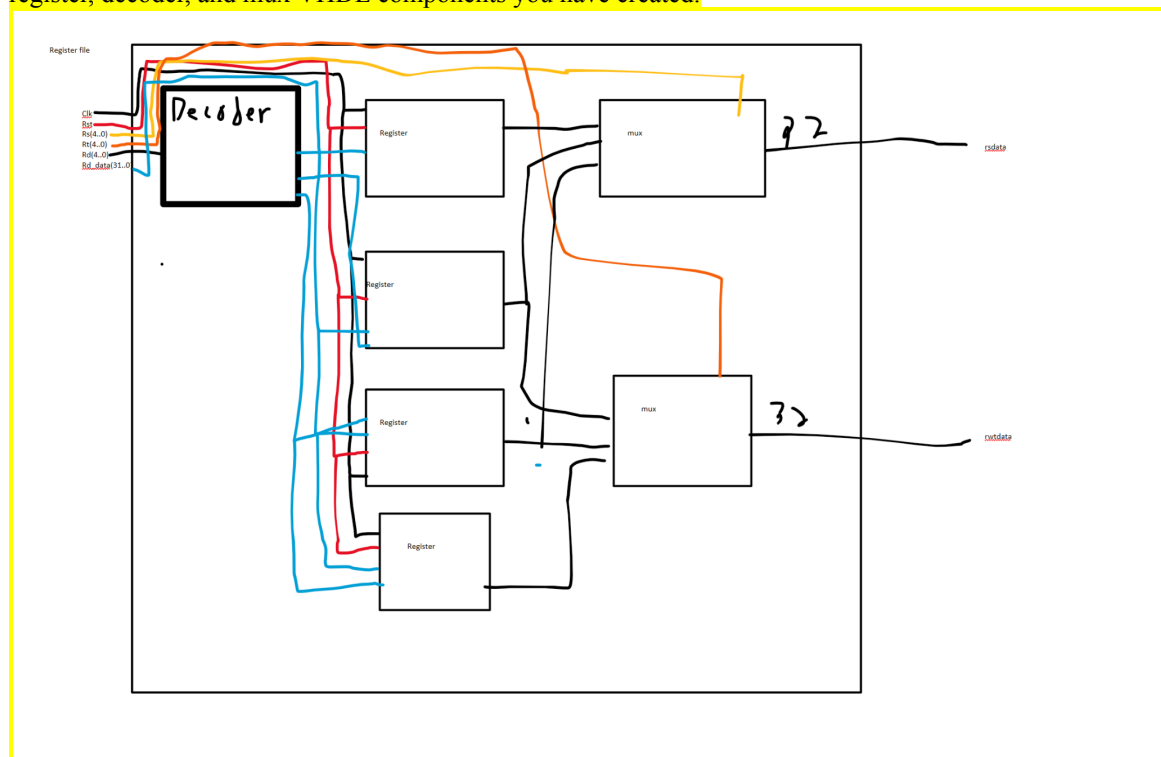
[Part 3 (h)] Draw a (simplified) schematic (i.e., components within the high-level blackbox) for the RISC-V register file, using the same top-level interface ports as in your solution describe above and using only the register, decoder, and mux VHDL components you have created.




[Part 3 (i)] Waveform.

 

 
[Part 4 (b)] Draw a symbol for this RISC-V-like datapath.



 [Part 4 (c)] Draw a schematic of the simplified RISC-V processor datapath consisting only of the component described in part (a) and the register file from problem (1).




 [Part 4 (d)] Include in your report waveform screenshots that demonstrate your properly functioning design. Annotate what the final state of the register file should be and provide a mapping of the registers used in your drawing to the register names.



[Part 5 (a)] Read through the mem.vhd file, and based on your understanding of the VHDL implementation, provide a 2-3 sentence description of each of the individual ports (both generic and regular).
DATA_WIDTH (generic): This generic sets the number of bits stored in each memory location (the word size). With the default value of 32, each address holds one 32-bit word, matching RV32 data width.
ADDR_WIDTH (generic): This generic sets the width of the address input and therefore the number of word locations in memory. The memory depth is 2^{ADDR_WIDTH} words, and in this lab the addresses index words, not bytes.
clk (port): The clock controls when writes occur in the RAM. When we='1', the memory writes data into the selected address on the rising edge of clk.
addr (port): This input selects which word of memory is being accessed. The output q reflects the contents at addr, so changing addr changes which word is read.
data (port): This is the value that will be written into memory during a store operation. It is only committed to memory on a rising clock edge when we='1'.
we (port): This write-enable signal determines whether a write happens on the next rising edge of clk. If we='0', memory contents are not modified.
q (port): This is the read-data output that reports the contents of the currently addressed word. It becomes valid once addr is stable (and after a write, it updates right after the clock edge that performs the write).

[Part 5 (c)] Waveforms and hex file.

 

[Part 6 (a)] What are the RISC-V instructions that require some value to be sign extended? What are the RISC-V instructions that require some value to be zero extended?

In risc v insturtations the 12-bit immediates used by I-type and S-type instructions are treated as signed values, so they must be sign-extended to 32 bits before being used (this includes addi, slti, xori, ori, andi, jalr, and the address offsets for loads/stores like lw/sw). For loads, the signed variants lb and lh also require sign extension of the loaded 8-bit or 16-bit value up to 32 bits. Zero extension is required when the loaded value is explicitly unsigned. The base instructions that do this are lbu and lhu, which zero-extend the 8-bit or 16-bit value to 32 bits.

[Part 6 (b)] what are the different 12-bit to 32-bit “extender” components that would be required by a RISC-V processor implementation?

A RISC-V processor needs extender hardware to expand 12-bit immediates into 32-bit values used by the datapath. At minimum, this means a 12→32 sign extender (replicating bit 11 into bits 31..12) for normal immediates and address offsets, and a 12→32 zero extender (filling bits 31..12 with zeros) for cases where the value is treated as unsigned. In practice, many designs implement this as a single extender module with a control bit that selects between sign-extend and zero-extend.

[Part 6 (d)] Waveform.

